



# Hardware Programming

## HWP01

capturing a  
FPGA  
design with  
VHDL

# Planning: theory

---

- First week
  - Introduction digital systems
  - Structured digital Design
  - RTL
- Second week
  - Introduction VHDL
  - Code structure and data types
  - Design verification
- **Third week**
  - Combinational versus sequential design
  - Concurrent and sequential code
  - Signals and variables
- Fourth week
  - Introduction to state machines
- Fifth week
  - Designing state machines
  - Advanced VHDL design


# Agenda

---



- **Discussion of previous week**
- Combinational versus sequential design
- Concurrent and sequential code
- Signals versus variables

# Numbers

# Bit Vectors

 

Zie ook:  
TABEL:  
H.3 ; blz 76

  

# Agenda


---

- Discussion of previous week
- **Combinational versus sequential design**
- Concurrent and sequential code
- Signals versus variables

# Combinational and sequential logic (1/2)

---


- Combinational: **no** memory

 

- The output is a function only of the current inputs.
- In any implementation there is a ***propagation delay***
  - For this course, we don't consider the propagation delay.

# Combinational and sequential logic (2/2)



- Sequential logic:

 

- The output of sequential logic, is ...  
... a function of a *sequence* of operations ..  
... on current and/or *previous inputs*.
- Advantages?



# Combinational vs. sequential logic example

- Combinational

  

Updates instantly as input changes (in theory).

- Sequential

  

Updates only when CLK goes high. Until then it remembers the previous input (memory)



# Combinational or sequential?

---

- Multiplexer vs. Synchronized Multiplexer?
- Timer?
- Encoder (for example binary to 7-seg display)?
- Comparators?
- Adder?
- Multiplier?
- ALU?
- CPU?
- Register?

# Agenda

---

- Discussion of previous week
- Combinational versus sequential design
- **Concurrent and sequential code**
- Signals versus variables


# Concurrent Code

---

- concurrent code is intended **only for combinational circuits**.
  - often used for structural descriptions of a circuit.
- outputs activated asynchronously, at any time.
- statements for concurrent code:
  - **when ... else**
  - **with ... select**
  - **generate**
- can be placed outside **process**, **function** and **procedure**

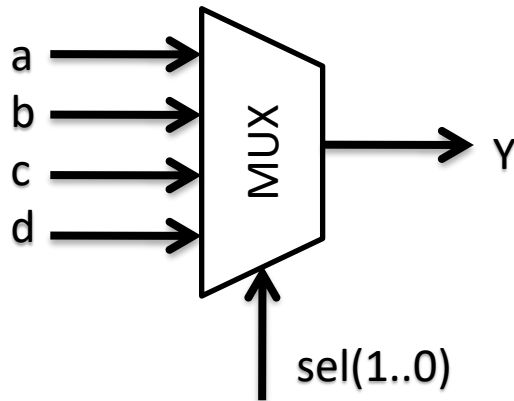
# WITH/SELECT

- **with ... select** is used very often
- read: depending on sel, y becomes a when sel is 00, y becomes b when sel is 01, etc...
- note the usage of the **others** keyword here to cover *all* possibilities



```
architecture mux2 of mux is
begin
  with sel select
    y <= a when "00",      -- use "," not ";"
        b when "01",
        c when "10",
        d when others;
end mux2;
```

# WHEN/ELSE

 


```
architecture mux1 of mux is
begin
    y <= a when sel="00" else
        b when sel="01" else
        c when sel="10" else
        d;
end mux1;
```


- Read: when sel is equal to "00", y obtains the value of a, else when sel is equal to "01", y obtains the value of b, etc...
- Cover all combinations
- Let the synthesizer do the K-map for us!
- Lijkt op een priority encoder

# Difference

- When/Else

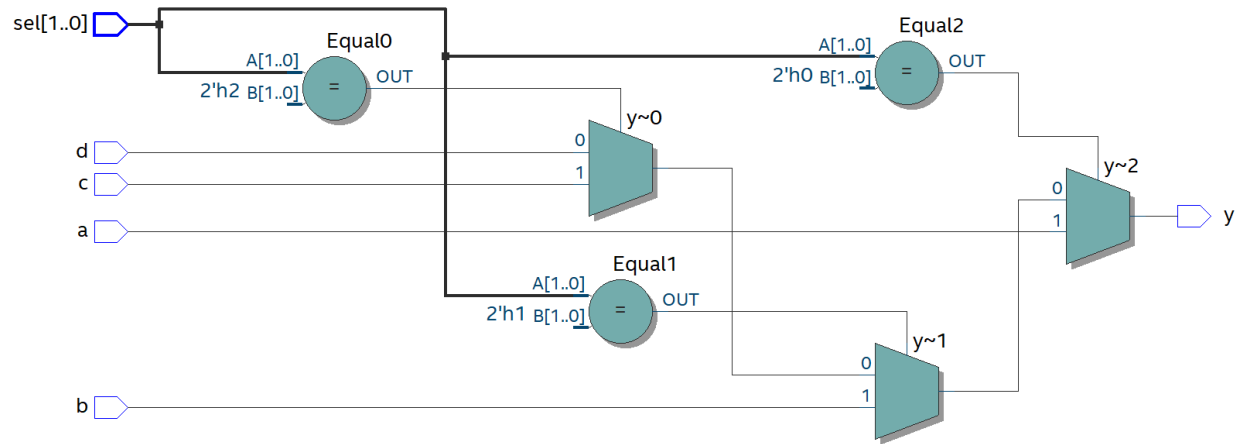


- With/Select

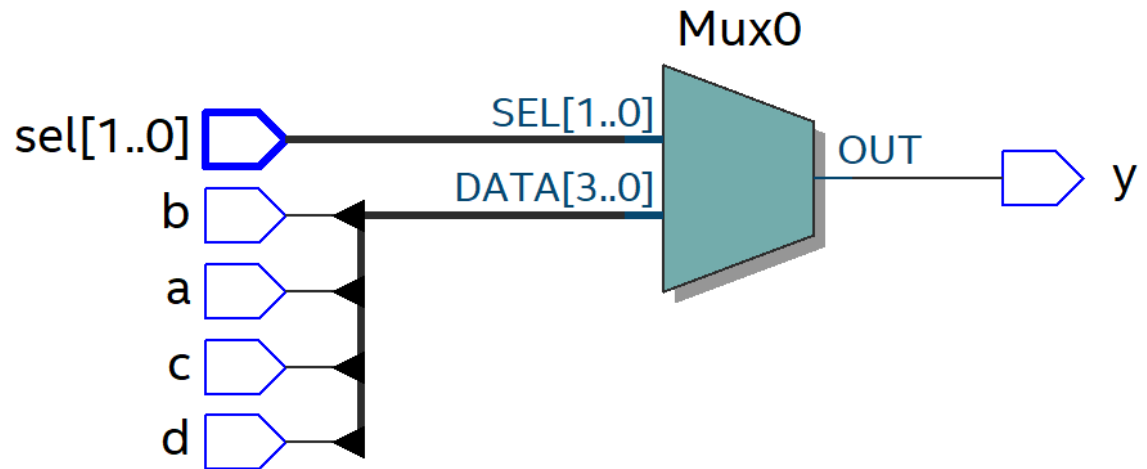
 
# Synchronized Multiplexer

```
library ieee;
use ieee.std_logic_1164.all;
-----
entity synced_mux is
    port (a, b, c, d, clk: in std_logic;
          sel      : in std_logic_vector (1 downto 0);
          y      : out std_logic);
end gated_mux;
-----
architecture behavioral of synced_mux is
    signal x: std_logic;
begin
    with sel select
        x <= a when "00",
        b when "01",
        c when "10",
        d when others;
-- use "," not ";"
process (clk)
begin
    if rising_edge(clk) then
        y <= x;
    end process
end architecture
```



# Sequential Code

---

- statements for sequential code:
  - **if**
  - **wait**
  - **loop**
  - **case**
- sequential code can be used to design both **sequential *and* combinational** circuits
- code within a **process, function** or **procedure** is sequential.







# Sequential Code


---

- **process** is a *sequential* section, located in the **architecture**
- note that multiple processes are allowed. they are *concurrent* to each other.
- support for the following *sequential* statements:
  - **if**
  - **wait**
  - **loop**
  - **case**
  - **with (since 2008)**
  - **when (since 2008)**

# Sequential Code Circuit Examples

 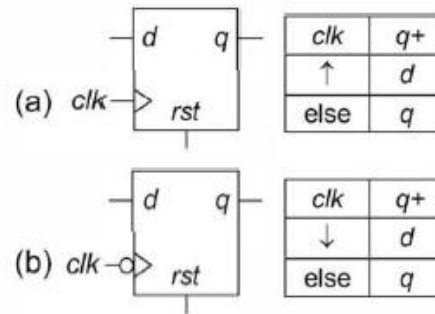 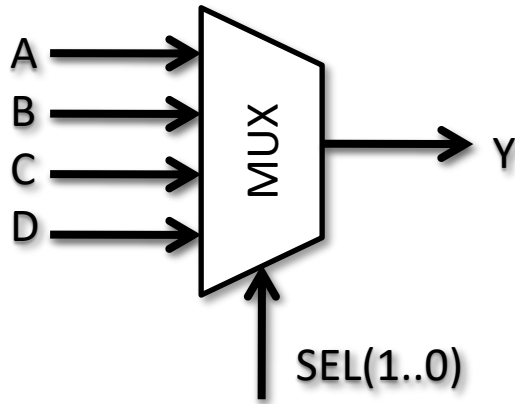

# Multiplexer with sequential code

 

- A **process** has a **sensitivity list**
- The outputs of the **process** get updated if the value of an object in the list changes


```
library ieee;
use ieee.std_logic_1164.all;
-----
entity seq_code_mux is
    port (a, b, c, d: in  std_logic;
          sel       : in  std_logic_vector (1 downto 0);
          y         : out std_logic);
end seq_code_mux;
-----
architecture seq_code_impl of seq_code_mux is
begin
    process (sel, a, b, c, d)
    begin
        if    sel = "00" then
            y <= a;
        elsif sel = "01" then
            y <= b;
        elsif sel = "10" then
            y <= c;
        else
            y <= d;
        end if;
    end process;
end seq_code_impl;
```

# Multiplexer with CASE


```
library ieee;
use ieee.std_logic_1164.all;
-----
entity seq_code_mux is
    port (a, b, c, d: in  std_logic;
          sel       : in  std_logic_vector (1 downto 0);
          y         : out std_logic);
end seq_code_mux;
-----
architecture seq_code_impl of seq_code_mux is
begin
    process(sel,a,b,c,d)
    begin
        case sel is
            when "00" =>
                y <= a;
            when "01" =>
                y <= b;
            when "10" =>
                y <= c;
            when others =>
                y <= d;
        end case;
    end process;
end seq_code_impl;
```

# Difference


- Case

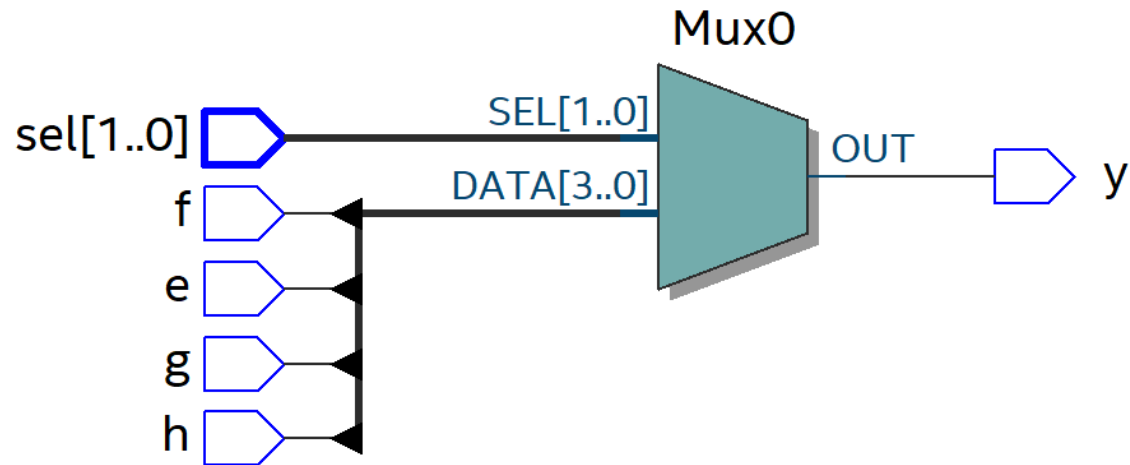

- If/Else

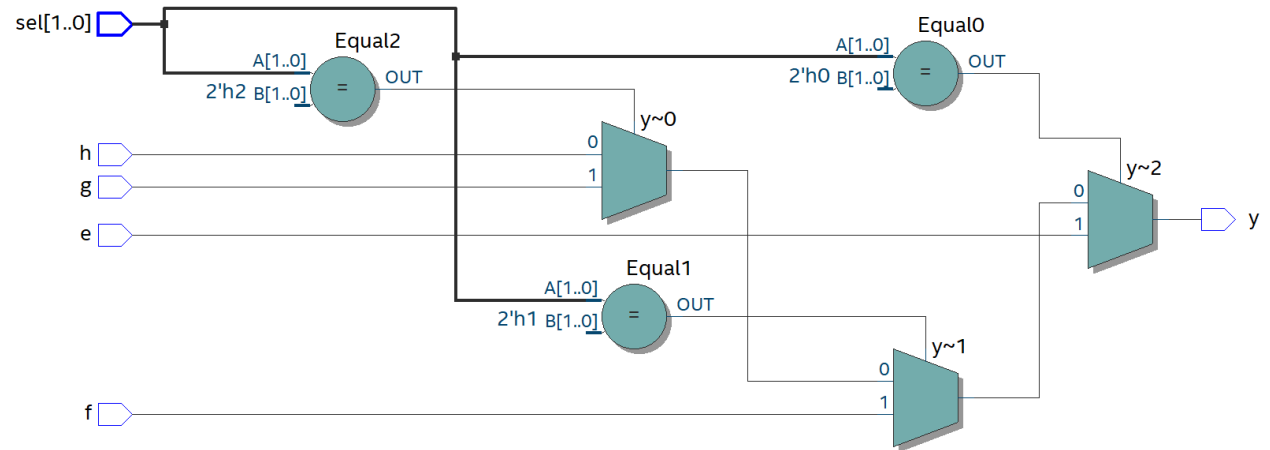

# D Flip-Flop

 


We only want to update Q when the CLK goes high, so only the CLK & R are in the sensitivity list

```
library ieee;
use ieee.std_logic_1164.all;
-----
entity dff_example is
    port (
        clk: in  std_logic;
        d,r: in  std_logic;
        q  : out std_logic
    );
end dff_example;
-----
architecture dff_implementation of dff_example is
begin
    process(clk, r )
    begin
        if r = '1' then
            q <= '0';
        elsif rising_edge(clk) then
            q <= d;
        end if;
    end process;
end dff_implementation;
```
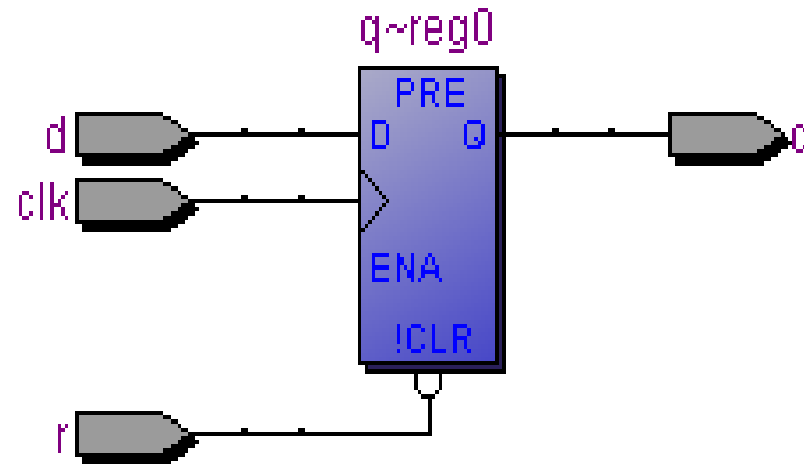
# Technology Map of DFF

Sequential circuits can only be written with sequential code



# Up/down counter

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;

entity updown is
    generic (
        counter_width : integer := 31
    );
    port (
        clk           : in std_ulogic;
        rst           : in std_ulogic;

        up_down      : in std_ulogic;


        count_out    : out std_ulogic_vector(counter_width downto 0)
    );
end updown;
```


 
# Up/down counter

```
architecture arch of updown is
    variable count : unsigned(counter_width downto 0);
begin
    process(clk)
    begin
        if rising_edge(clk) then
            if rst = '1' then
                count <= (others => '0');
            else
                if up_ndown = '1' then
                    count <= count + 1;
                else
                    count <= count - 1;
                end if;
            end if;
        end if;
    end process;

    count_out <= std_ulogic_vector(count);
end arch;
```



# WAIT

---

- In a **process** you can use the **wait** keyword
- A process CANNOT have both a sensitivity list and **wait** statements
- Three types:
  - **wait until** *condition*
  - **wait on** *sig1, sig2, ..., sign* (sensitivity list)
  - **wait for** *time*
- **wait for** cannot be synthesized; only for simulation and test benches

# D Flip-Flop with WAIT


```
LIBRARY ieee;
USE ieee.std_logic_1164.all;

-----

ENTITY dff_example IS
    PORT (
        clk: IN  STD_LOGIC;
        d,r: IN  STD_LOGIC;
        q  : OUT STD_LOGIC
    );
END dff_example;

-----

 ARCHITECTURE dff_implementation OF dff_example IS
BEGIN
    PROCESS
    BEGIN
        WAIT UNTIL RISING_EDGE(clk);
        q <= d;
    END PROCESS;
END dff_implementation;
```



Not very  
handy without  
a reset ☹️

# Loops in VHDL

---

- **for** and **while** loops
- **for ... loop** repeats until the upperbound is reached
- static bounds; use constants to specify the upper bound of your loop

```
process(sel)
  ..
  begin
    for i in 0 to 5 loop
      x <= i;
    end loop;
  end process;
```

# Loops in VHDL

---

- **while ... loop** is similar in structure as the **for ... loop**
- see page 161 of your book for some examples with loops

```
process(sel)
..
begin
while i<10 loop
...do something...
end loop;
end process;
```

# Agenda

---

- Discussion of previous week
- Combinational versus sequential design
- Concurrent and sequential code
- **Signals versus variables**

# Signals versus variables

---

- **SIGNAL**

- Is eigenlijk een verbinding of draadje
- Bedoeld om data over te brengen tussen verschillende blokken zoals concurrent statements en processen

- **VARIABLE**

- Is meer een abstracte waarde
- Het wordt gebruikt om iets te onthouden binnen een process

# Signals versus variables

---

- **SIGNAL** properties:
  - Can *ONLY* be declared outside a **process** but can be used within a **process**
  - Within sequential code the signal is not ‘updated immediately’ (at the end of the **process**)
  - Only a *single* assignment is allowed to a signal in the whole code (multiple assignments in **processes** are fine, but only the last one will be effective!)
- **VARIABLE** properties:
  - Can *ONLY* be declared inside a **process**
  - Is ‘updated immediately’ and can be used in the next line of code
  - *Multiple* assignments are not a problem



# Summary

---

- Combinational versus sequential design: no memory versus memory.
- In VHDL we can model combinational circuits with sequential statements
- Remember the differences between signals and variables

# Homework

---

- Covered today:
  - Discussion of previous week
  - Combinatorial versus sequential design
  - Concurrent and sequential design
  - Signals versus variables
  
- Next week:
  - Chapter 12 (13) 'Sequential Code'
    - ! Chapter 12.9 'SIGNAL and VARIABLE'
  - Chapter 14.3 – 14.5 'FUNCTION and PROCEDURE'