



Hardware Programming

HWP01

capturing a
FPGA
design with
VHDL

Fifth Week: Theory



- Theory:
 - Ch15+16: State Machines
- Goals:
 - Learn how to design and implement a Finite State Machine in a digital circuit using VHDL

Agenda


- **Finite State Machines**
- Example
- Example in VHDL
- Template in VHDL

Finite State Machines Design

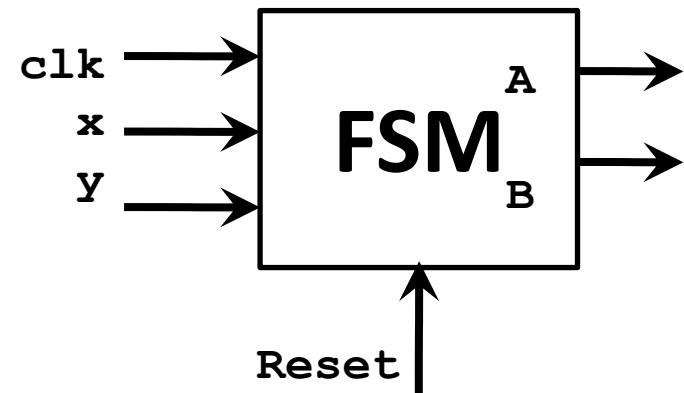 
- FSM diagrams consist of:
 - States
 - Transitions
 - Conditions
 - Inputs
 - Outputs
 - Reset



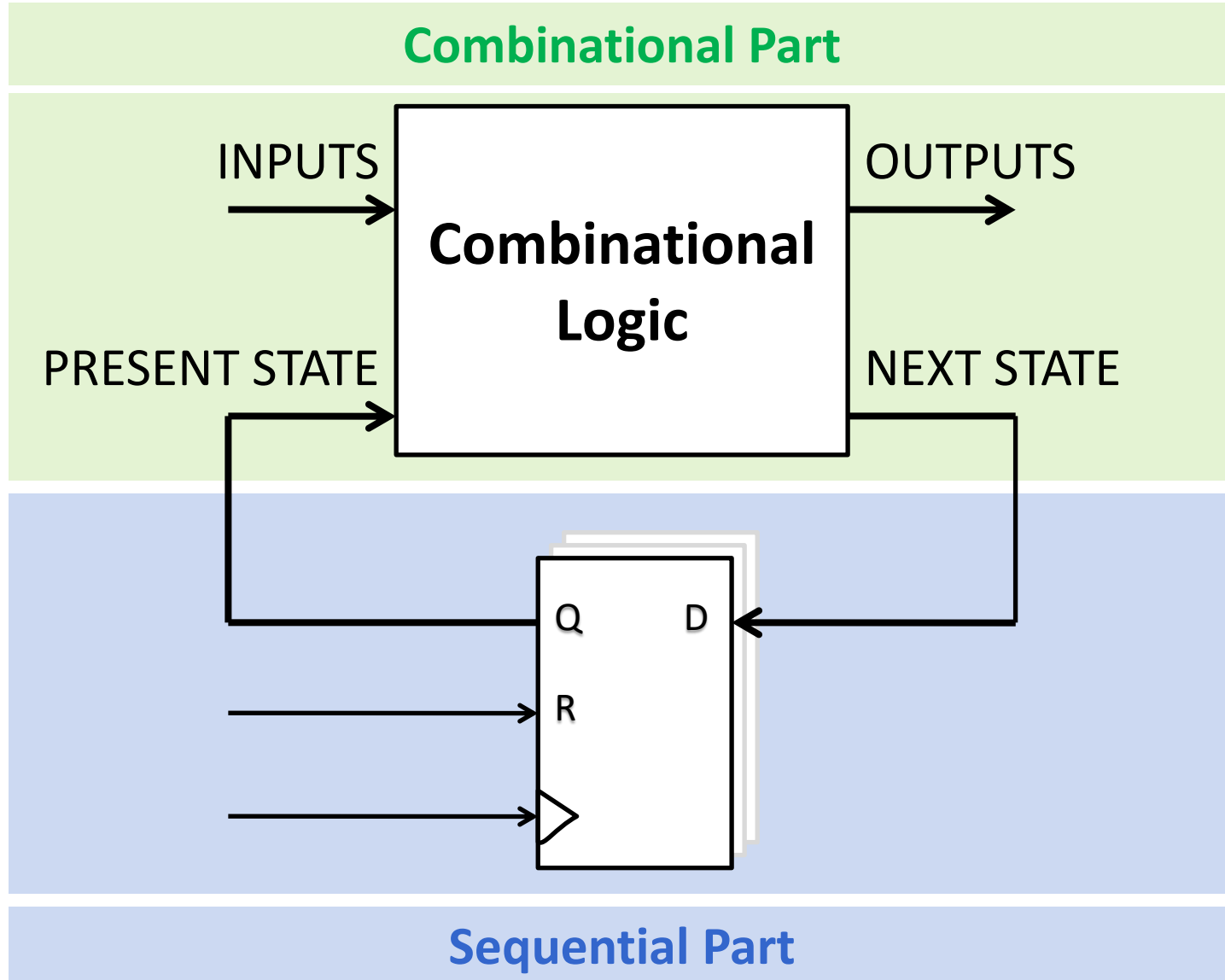Finite State Machines in Digital Circuits




The Sequential Part

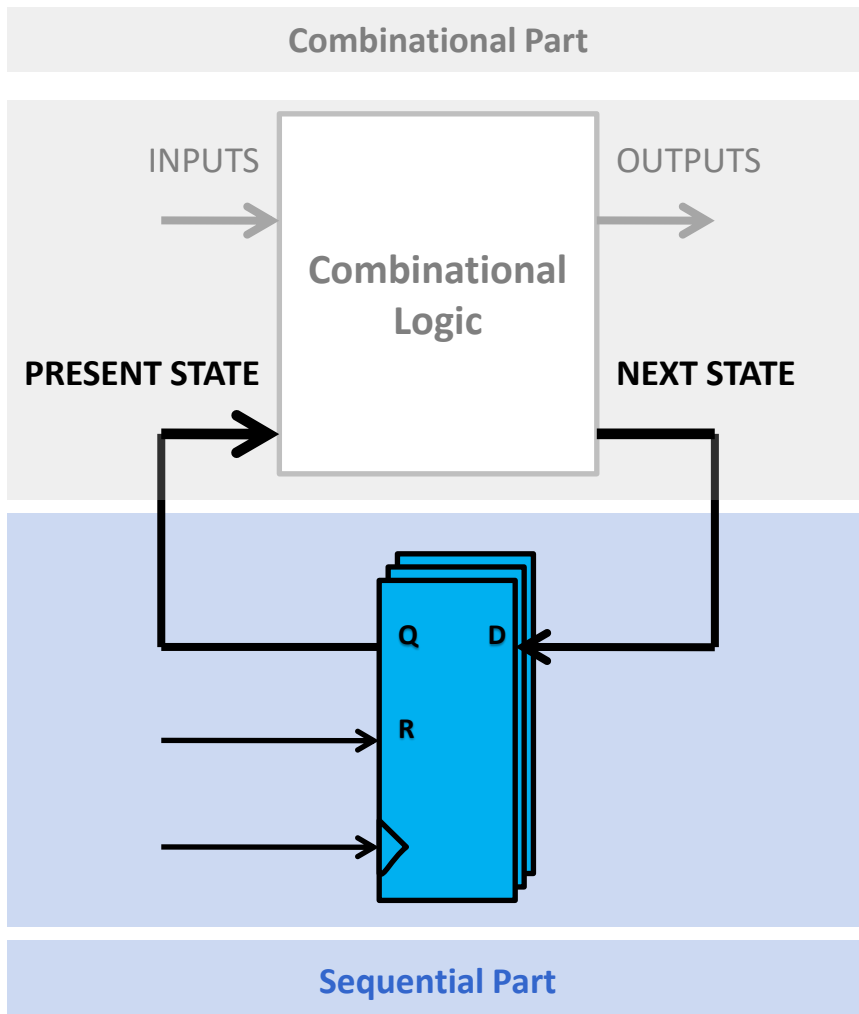


- The sequential part consists only of **dffs**, a **clock** and a **reset**.
- The flip-flops hold the **present state**
- They switch to the **next state** on the **clock-edge**
- The **reset** makes the **present state** 0000 (initial state).
- The **combinational** part determines the **next state** by the **inputs** and **present state**

Encoding the State Bus

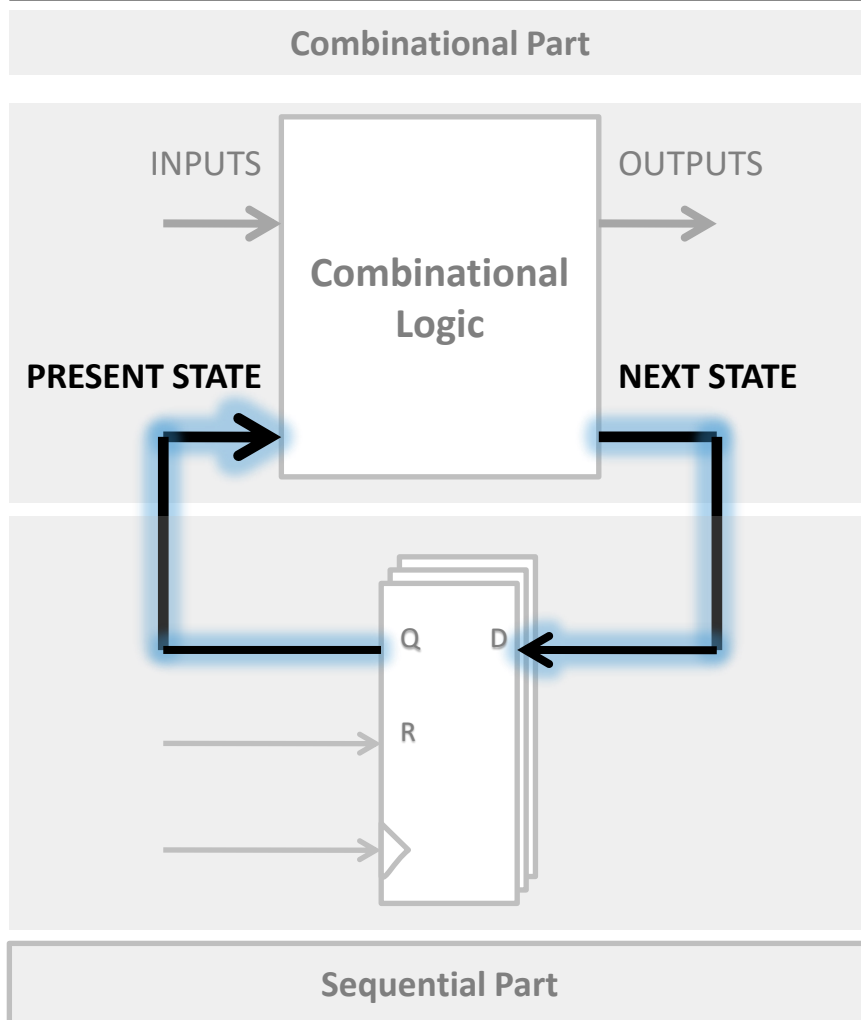

- The states are represented by bits (of course)
- Encoding states can be done in a few ways:
 - State BINARY GRAY ONE-HOT
 - 0 00 00 0001
 - 1 01 01 0010
 - 2 10 11 0100
 - 3 11 10 1000
- Why? (See Ch. 2.6.5)
- Keep it easy, let Quartus decide the encoding.
- See Ch. 15.2 how to do this.


The Combinational Part

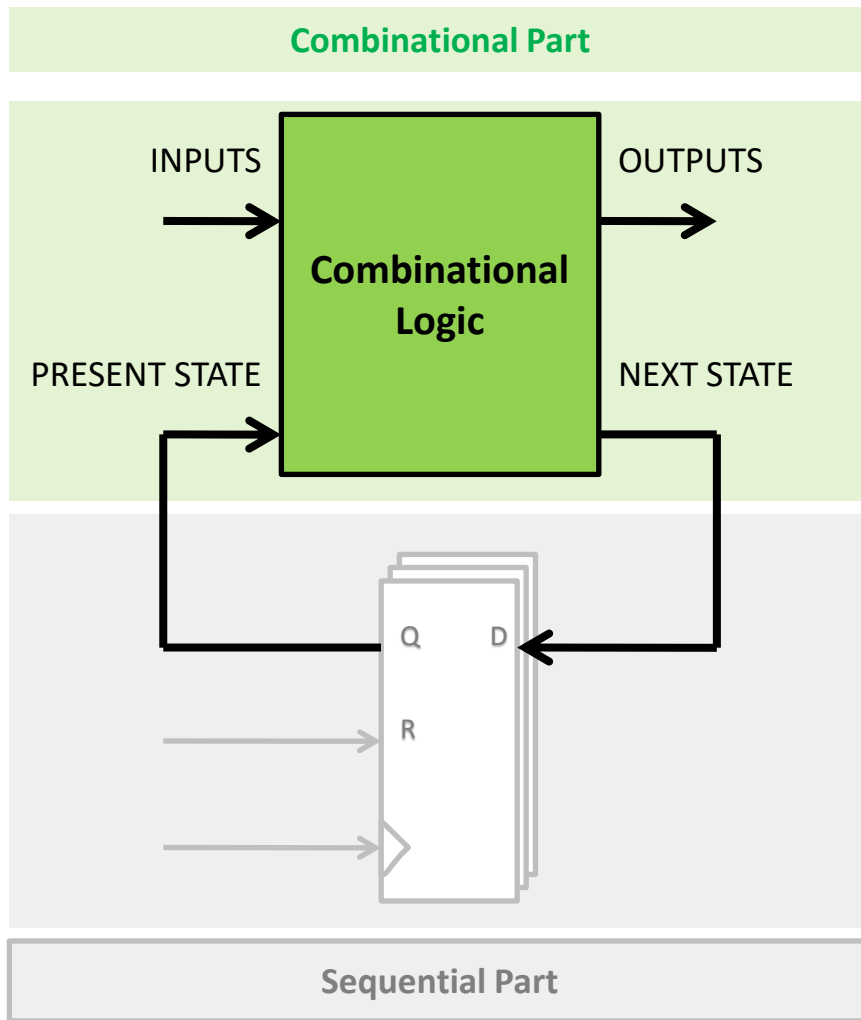

- the combinational part determines the **next state**
 - it is a function of the inputs and present state
- the combinational part determines the **outputs**
 - Moore: it is a function of the present state
 - Mealy: it is a function of the present state combined with the inputs
- Always design as Moore and change to Mealy if output needs to react instantly

- Template M1 on page 382
- [Listing](#)

The Combinational Part

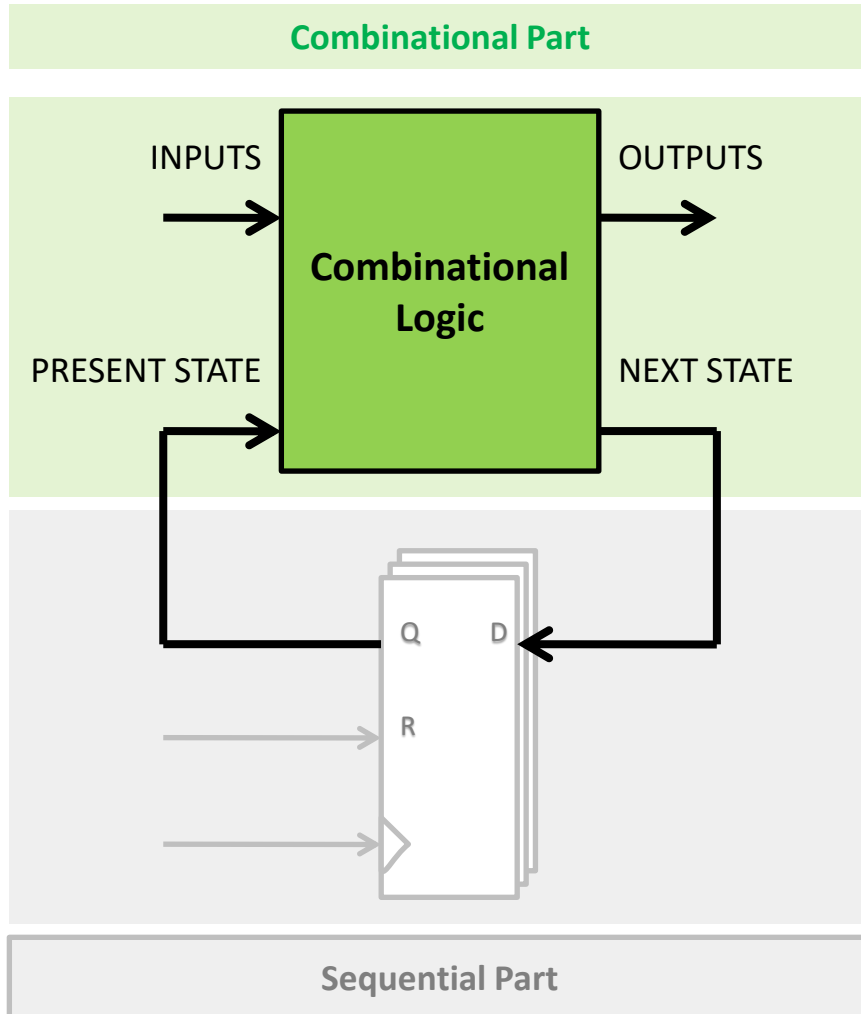


- The Combinational Part is Combinational Logic
- It is a (simple) Boolean Function
- We can draw a truth-table for this
- We can use K-maps to minimize the logic


Agenda

- Finite State Machines
- **Example**
- Example in VHDL
- Template in VHDL

Egg Timer: FSM Context

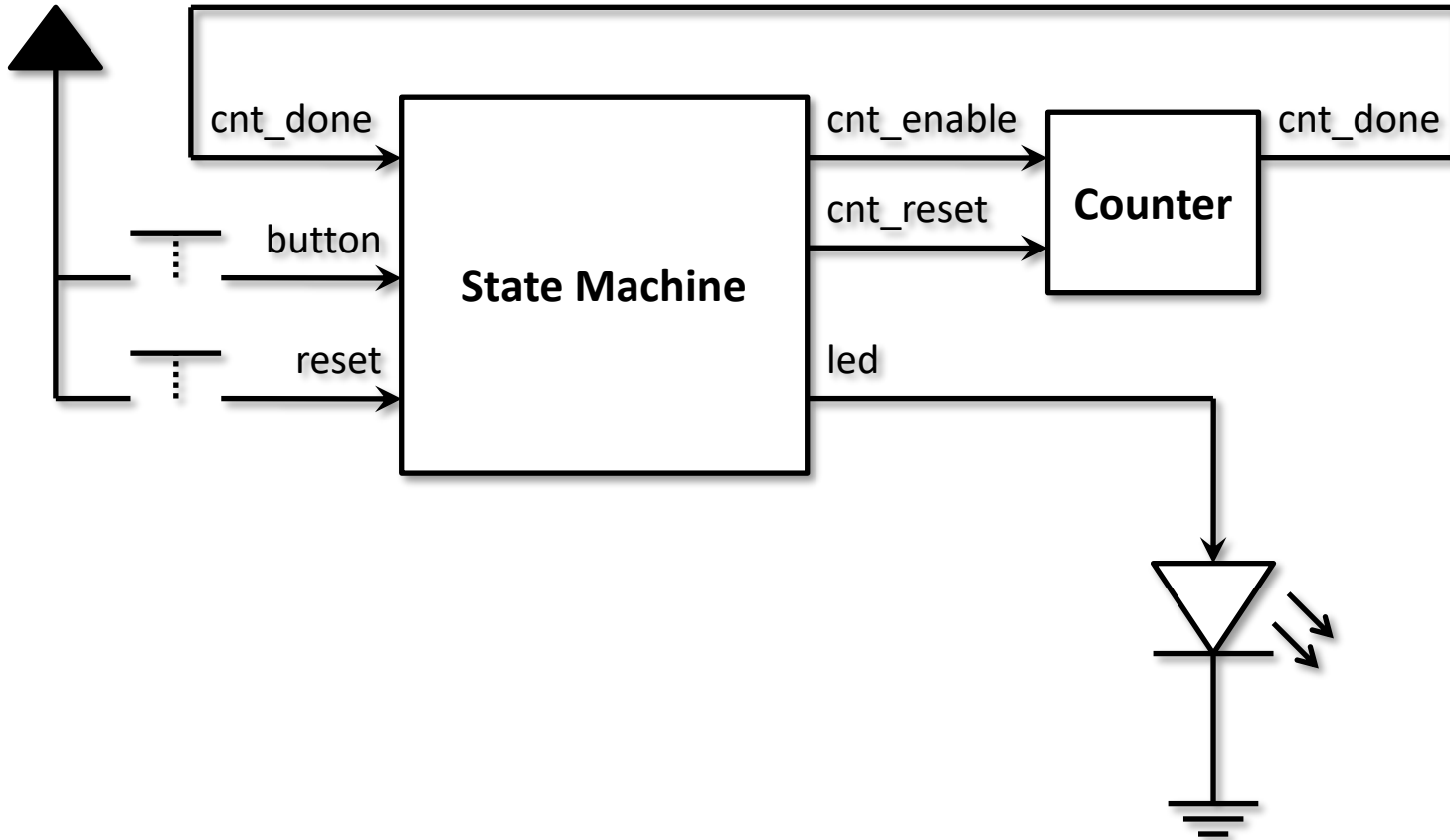

Egg Timer: State Diagram

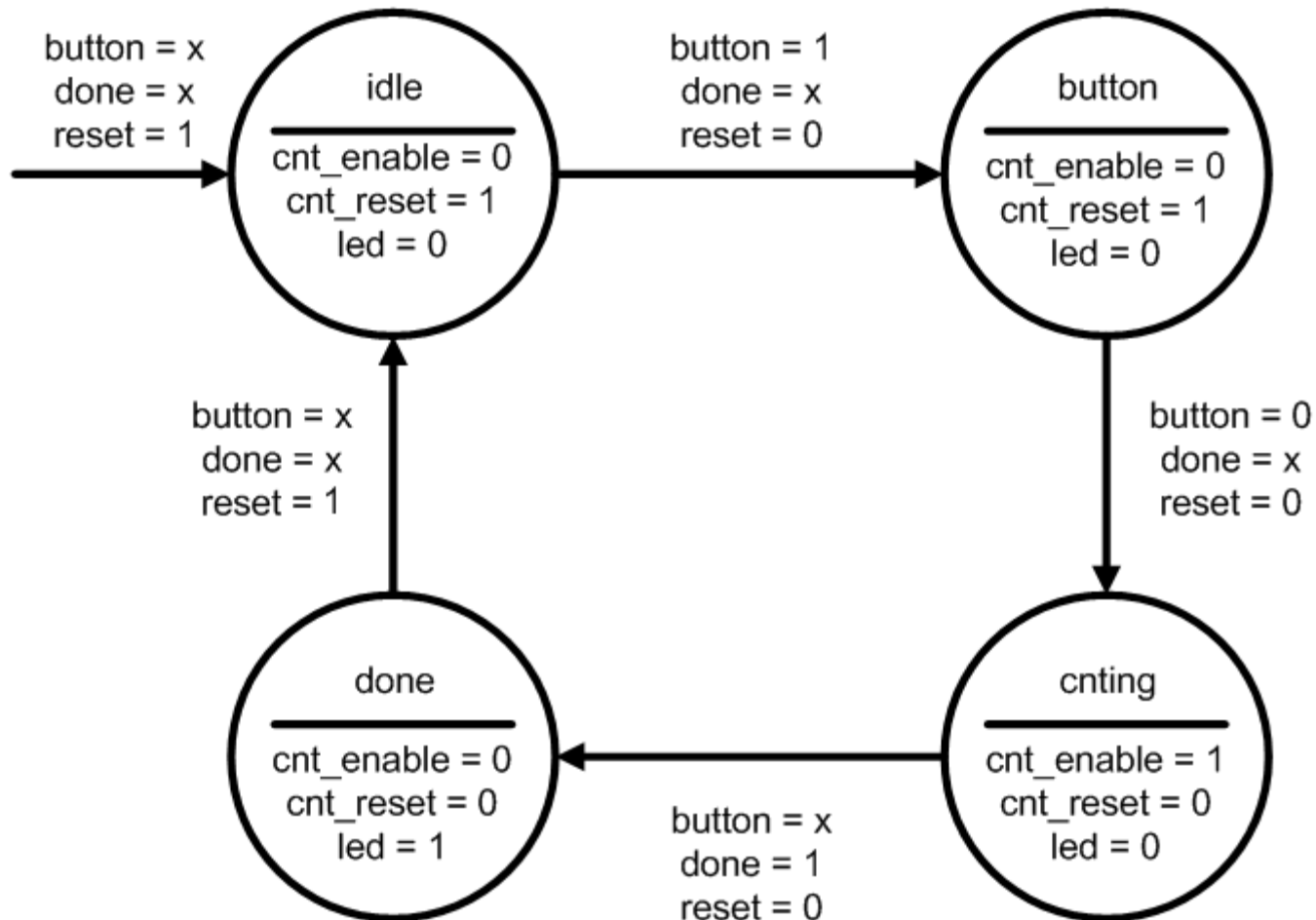

Agenda

- Finite State Machines
- Example
- **Example in VHDL**
- Template in VHDL

Example in VHDL

- Same Egg Timer: the entity

```
library ieee;
use ieee.std_logic_1164.all;

entity fsm_egg_timer is
    port(
        clk, reset, btn, cnt_done : in std_ulogic;
        cnt_enable, cnt_reset, led : out std_ulogic
    );
end entity;
```

State Bus Encoding in VHDL

- We need to define the states inside our architecture.
- We can use the “TYPE” keyword, it’s like “ENUM” in C. The synthesizer will define what idle, button, cnting, etc... is.
- We need to define signals for the present and next state.

```
architecture rtl of fsm_egg_timer is

    -- Define an enumerated type for the state machine
    type state_type is (idle, button, cnting, done);

    -- Register to hold the current state
    signal present_state, next_state : state_type;

begin
```

Define the flip-flops

```
-- state register
pr_flipflops : process (clk, reset)
begin
    if reset then
        present_state <= idle;
    elsif rising_edge(clk) then
        present_state <= next_state;
    end if;
end process;
```

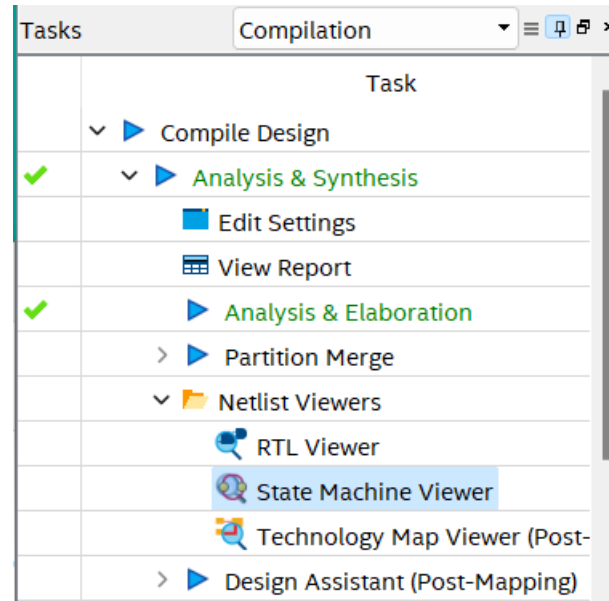

Write the transitions

```
-- logic to determine the next state
pr_next_state : process (present_state, btn, cnt_done)
begin
    case present_state is
        when idle =>
            if btn then
                next_state <= btn;
            else
                next_state <= idle;
            end if;
        when btn =>
            if not btn then
                next_state <= cnting;
            else
                next_state <= btn;
            end if;
        when cnting =>
            if cnt_done then
                next_state <= done;
            else
                next_state <= cnting;
            end if;
        when done =>
            next_state <= done;
    end case;
end process;
```

Write the outputs (Moore)

```
-- Logic to determine the outputs
pr_outputs: process (present_state)
begin
    case present_state is
        when idle =>
            cnt_enable <= '0';
            cnt_reset  <= '1';
            led        <= '0';
        when btn =>
            cnt_enable <= '0';
            cnt_reset  <= '1';
            led        <= '0';
        when cnting =>
            cnt_enable <= '0';
            cnt_reset  <= '0';
            led        <= '0';
        when done =>
            cnt_enable <= '1';
            cnt_reset  <= '0';
            led        <= '1';
    end case;
end process;
end architecture;
```

State Machine Viewer



- Quartus can detect a state machine in your code!

State Machine Viewer

The screenshot shows the State Machine Viewer interface. The title bar reads "State Machine Viewer - C:/HWP01/fsm_sheets/fsm_sheets - fsm_egg_timer". The menu bar includes "File", "Edit", "View", "Tools", "Window", and "Help". A search bar contains "Search altera.com". The main area displays a state transition diagram with four states: "idle", "button", "cnting", and "done". Each state is represented by a yellow circle with a self-loop arrow. Transitions are shown as curved arrows between states: "idle" to "button" on "btn", "button" to "cnting" on "cnt", "cnting" to "done" on "cnt", and "done" to "idle" on "reset".

Below the diagram is a "State Table" with the following data:

	Source State	Destination State	Condition
1	button	cnting	(!btn)
2	button	button	(btn)
3	cnting	cnting	(!cnt_done)
4	cnting	done	(cnt_done)
5	done	done	
6	idle	button	(btn)
7	idle	idle	(!btn)

The interface also shows tabs for "Transitions" and "Encoding", and a status bar at the bottom right with "100%" and "00:00:01".

Agenda

- Finite State Machines
- Example
- Example in VHDL
- **Template in VHDL**

Write the outputs (Moore)

```
library ieee;
use ieee.std_logic_1164.all;

entity fsm is
    port (
        clk, rst: in std_ulogic;
        input1, input2, ...: in std_ulogic;
        output1, output2, ...: out std_ulogic
    );
end fsm;

architecture behavior of fsm is
    type state_type is (idle, state1, state2,
...);
    signal pr_state, nx_state: state_type;
begin

    process(clk, rst)
    begin
        if rst then
            pr_state <= idle;
        elsif rising_edge(clk) then
            pr_state <= nx_state;
        end if;
    end process;
```

```
        process(pr_state, input1, input2, ...)
        begin
            case pr_state is
                when idle =>
                    if input1 then
                        nx_state <= state1;
                    else
                        nx_state <= state2;
                    end if;
                when state1 =>
                    nx_state <= state2;
                when state2 =>
                    ...;
                when ... =>
                    ...;
            end case;
        end process;

        process(pr_state)
        begin
            case pr_state is
                when idle =>
                    output1 <= '0';
                    output2 <= '0';
                    ...
                when state1 =>
                    output1 <= '0';
                    output2 <= '1';
                    ...
                when state2 =>
                    ...;
                when ... =>
                    ...;
            end case;
        end process;
    end architecture;
```

- Template M1 on page 382
- [Listing](#)

Advantages of using the template

- Readability
- Reusability
- Adaptability
- Quicker (especially for bigger designs)

- Quartus also has built-in templates (right-click in the editor)